

# BUNAMFAN CLUSTER EXAMINATION - 2022

Kenya Certificate of Secondary Education

448/1 – ELECTRICITY (*Theory*)– Paper 1

June 2022 - 2 ½ hours

Name.....Adm No.....

Class..... Date.....

## INSTRUCTIONS TO CANDIDATES

Candidates should have the following for this examination

1. Mathematical tables or non-programmable calculators may be used
2. This paper has TWO sections: **A** and **B**
3. Answer **ALL** the questions in section **A** and **ANY FOUR** questions from section **B**.
4. All dimensions are in millimeters unless stated otherwise.
5. This paper consists of **11** Printed pages.
6. Candidates should check the question paper to ensure that all the Papers are printed as indicated and no questions are missing

visit [www.freekcsepastpapers.com](http://www.freekcsepastpapers.com) to download free resources.

*This paper consists of 9 Printed pages.  
Candidates should check the question paper to ensure that all the  
Papers are printed as indicated and no questions are missing*

**SECTION A** (48 marks)

*Answer all the questions in this section in the spaces provided*

1. (a) List **four** insulating materials used in electrical installations. (2 marks)

.....  
.....  
.....  
.....  
.....

- (b) State **two** advantages of mineral insulated copper sheathed cables over PVC sheathed. (2 marks)

.....  
.....

2. (a) State Lenz's law of electromagnetic induction. (2 marks)

.....  
.....

- (b) Name **four** applications of electromagnets. (2 marks)

.....  
.....  
.....  
.....

3. (a) Name **four** National Polytechnics in Kenya. (2 marks)

.....  
.....  
.....  
.....

- (b) List **two** business opportunities in the field of electricity. (1 mark)

.....  
.....  
.....  
.....

4. (a) State how each of the following electrical material waste should be disposed safely:  
(i) Burnt fluorescent tubes; (½ mark)

.....  
.....

(ii) Damaged computers. (½ mark)

.....  
.....


(b) State the application of each of the following types of extinguishers:  
(i) Carbon dioxide; (1 mark)

.....  
.....


(ii) Water. (1 mark)

.....  
.....

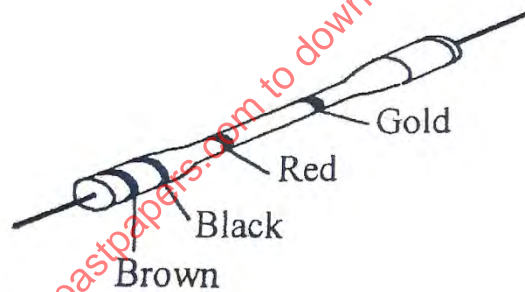5. (a) **Figure 1** shows a carbon resistor with color codes. Determine the value of the resistor given, (2 marks)



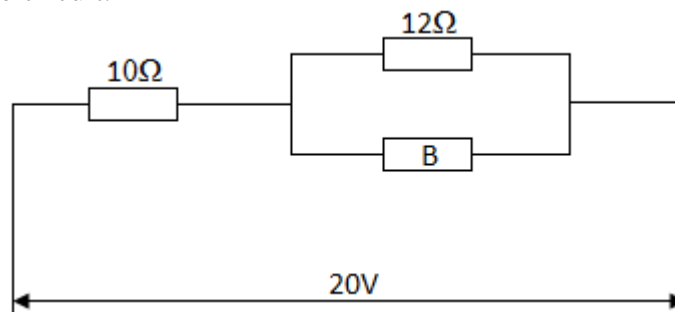6. **Figure 2** shows a resistive circuit.



Determine the:

(a) Value of the resistor **B** if the total circuit resistance is 20Ω; (4 marks)

(b) Total circuit current. (2 marks)


7. (a) Name **four** parts of a fluorescent fitting. (2 marks)

.....  
.....  
.....  
.....


(b) List four marking out tools used in fabricating sheet metal casing. (2 marks)

.....  
.....  
.....  
.....

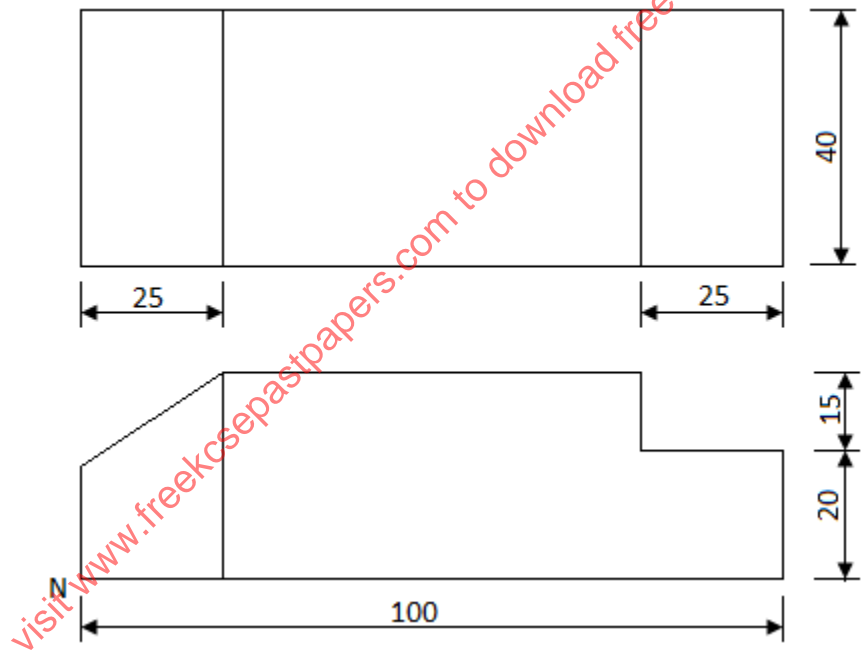8. (a) **Figure 3** shows two views of an object drawn in third angle projection.



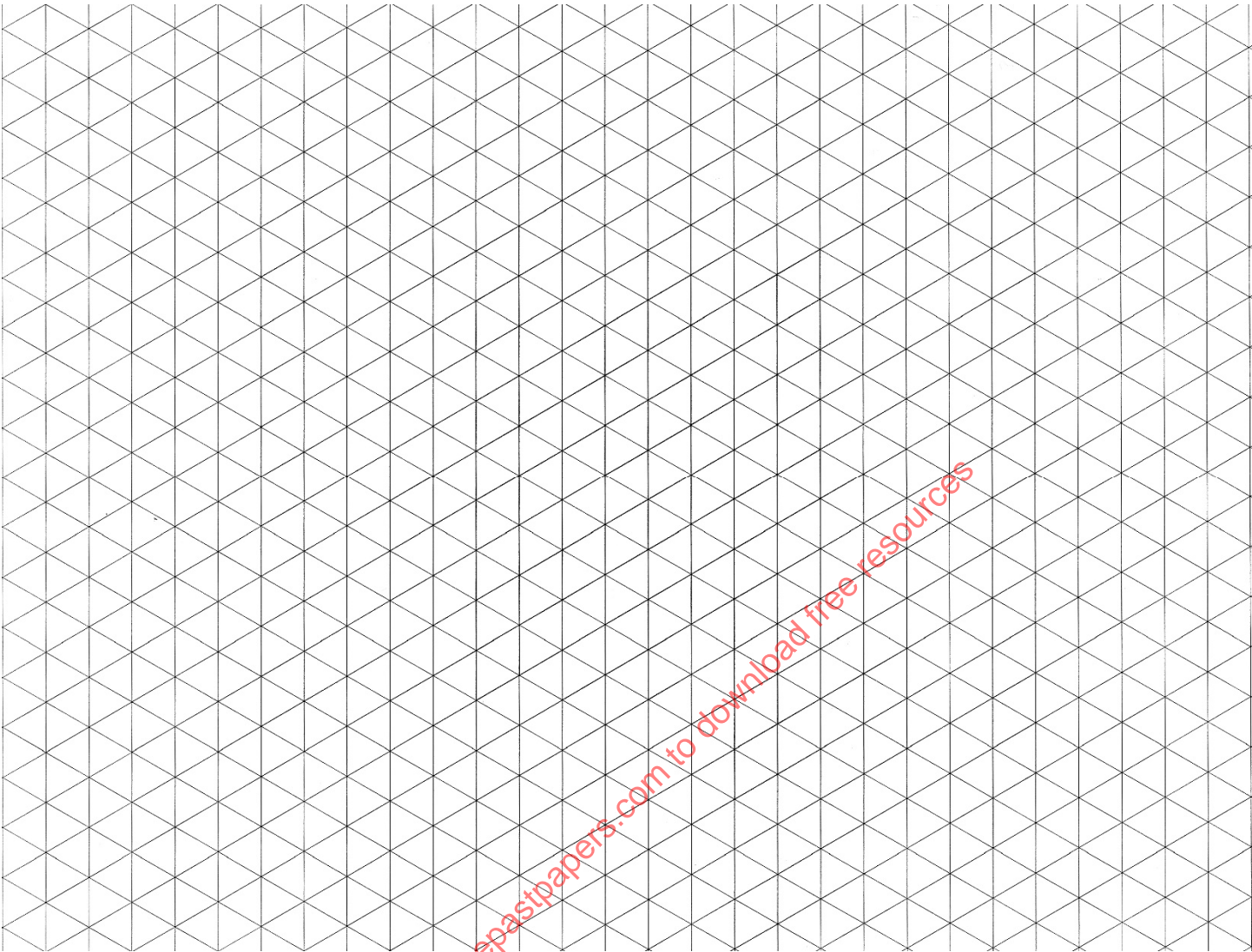On the grid provided, make a free hand isometric sketch with corner N as the lowest point. (3 marks)



visit [www.freekcsepastpapers.com](http://www.freekcsepastpapers.com) to download free resources

(b) Outline **two** ways that can be used to troubleshoot a faulty television. (2 marks)

.....  
.....

9. (a) With the aid of sketches, distinguish between P-N-P and an N-P-N transistor. (3 marks)

(b) Name **four** applications of a P-N junction diode. (2 marks)

.....  
.....  
.....  
.....

10. (a) State three advantages of digital instruments over analogue instruments. (3 marks)

.....  
.....  
.....  
.....

(b) An ideal transformer connected to a 240V mains supplies a 12V, 120W lamp. Calculate the:

(i) Transformer's turns ratio; (3 marks)

(ii) Current taken from the supply. (3 marks)

*visit [www.freekcsepastpapers.com](http://www.freekcsepastpapers.com) to download free resources*

**SECTION B** (52 marks)

*Answer any four questions in the spaces provided.*

11. (a) (i) Convert  $23_{10}$  to binary. (2 marks)

(ii) Convert  $11011_2$  to decimal. (2 marks)

(b) Draw a truth table for each of the following logic gates: (4 marks)  
(i) NOR;

(ii) NAND. (4 marks)

(c) Name two applications of logic gates. (1 mark)

.....  
.....  
.....


visit [www.freekcsepastpapers.com](http://www.freekcsepastpapers.com) to download free resources

12. (a) Draw a sine wave and indicate the following:

- (i) Peak value;
- (ii) Instantaneous value;
- (iii) Cycle.

(5 marks)

(b) **Figure 4** shows an RLC circuit.

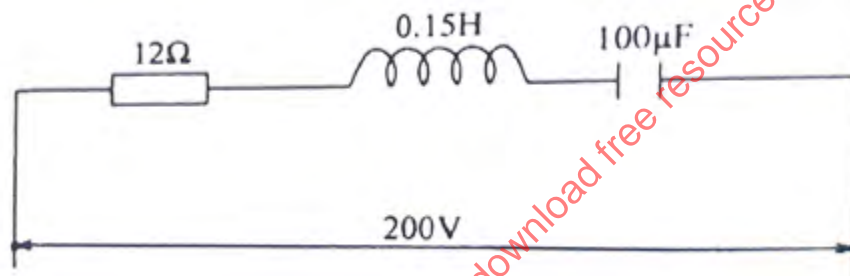

Calculate the:

(i) Inductive reactance;

(2 marks)

(ii) Capacitive reactance;

(2 marks)

(iii) Circuit impedance;

(2 marks)

(iv) Circuit current.

(2 marks)



13. (a) State;  
(i) **Two** advantages of a moving coil instrument. (2 marks)

.....  
.....  
.....

- (ii) **Two** essential features of an analogue instrument. (2 marks)

.....  
.....  
.....

- (b) With the aid of a labelled diagram, explain the Flemmings right hand rule to demonstrate the direction of induced EMF. (6 marks)

- (c) show that for two capacitors  $C_1$  and  $C_2$  connected in series, the total capacitance is given by:

$$C_T = \frac{C_1 \times C_2}{C_1 + C_2}$$

(3 marks)

visit [www.freejsepastpapers.com](http://www.freejsepastpapers.com) to download free resources

14. (a) State:  
(i) **Two** advantages of trunking over steel conduit wiring systems. (2 marks)

.....  
.....  
.....

(ii) **Two** advantages of MCBs over rewirable fuses. (2 marks)

.....  
.....  
.....


(b) (i) Draw and label a diagram of a switch start fluorescent fitting. (6 marks)

(ii) Outline **three** tests carried out in a completed electrical installation. (3 marks)

.....  
.....  
.....  
.....  
.....  
.....

visit [www.freekcsepastpapers.com](http://www.freekcsepastpapers.com) to download free resources

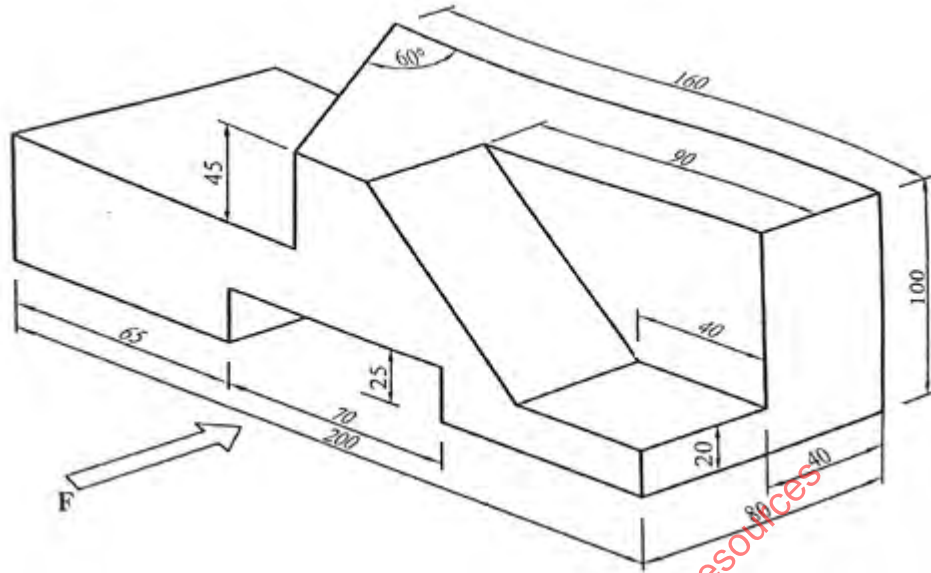15. **Figure 5** shows a machine block drawing of an isometric projection.



Draw the following views in **full size** in first angle projection:

- (a) Front elevation in the direction of arrow **F**;
- (b) Plan;
- (c) Indicate **six** dimensions.

(13 marks)

visit [www.freekcepastpapers.com](http://www.freekcepastpapers.com) to download free resources

**THIS IS THE LAST PRINTED PAGE**